


ELC4438: Embedded System Design

Finite State Machine for RISC SPM


Liang Dong

Electrical and Computer Engineering
Baylor University

Partitioned Sequential Machine

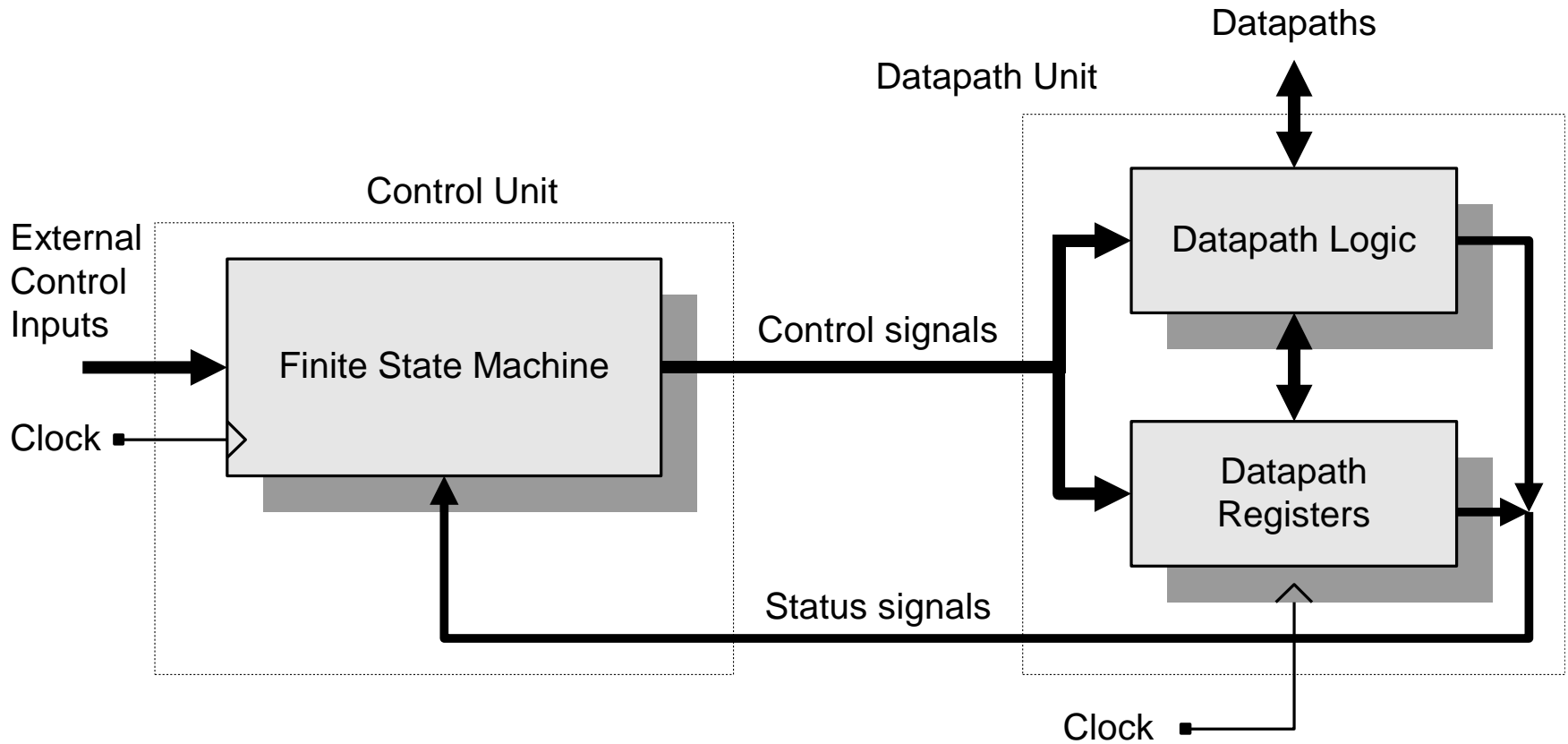


Application-Driven Architecture

 

Design Example – Binary Counter


- Synchronous 4-bit binary counter
- Incremented by a count of 1 at each active edge of the clock
 - *enable* must be asserted for counting to occur
 - *rst* overrides all activity and drives the count to a value of *0000*.
- Wrap count to 0 when the count reaches 1111_2 .
- Functional elements of the architecture of the datapath unit:
 - 4-bit register to hold *count*,
 - mux that steers either *count* or the sum of *count* and 1 to the input of the register
 - a 4-bit adder to increment *count*

Binary Counter Architecture

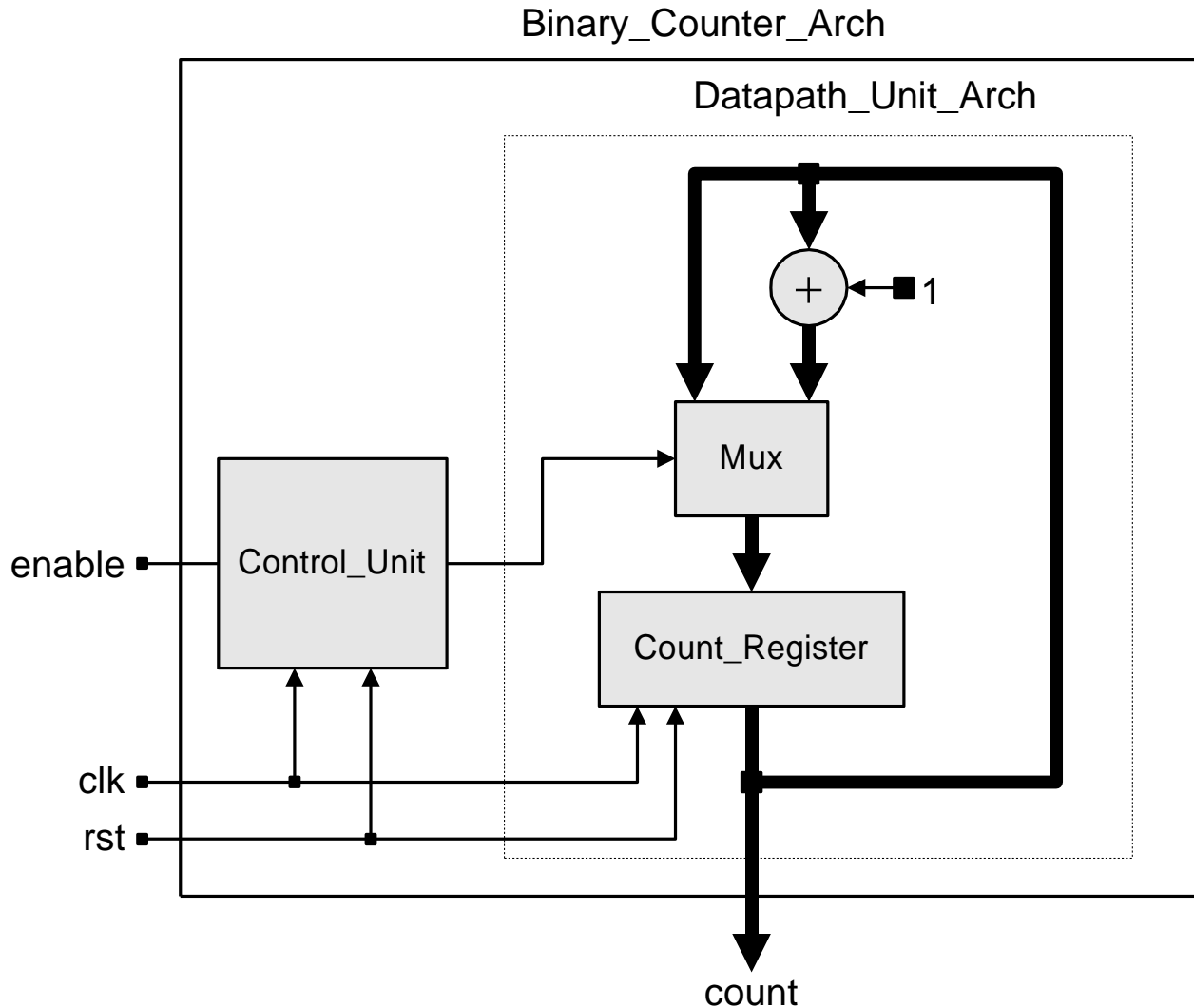

Alternative Counter Design

- Explicit Finite State Machine

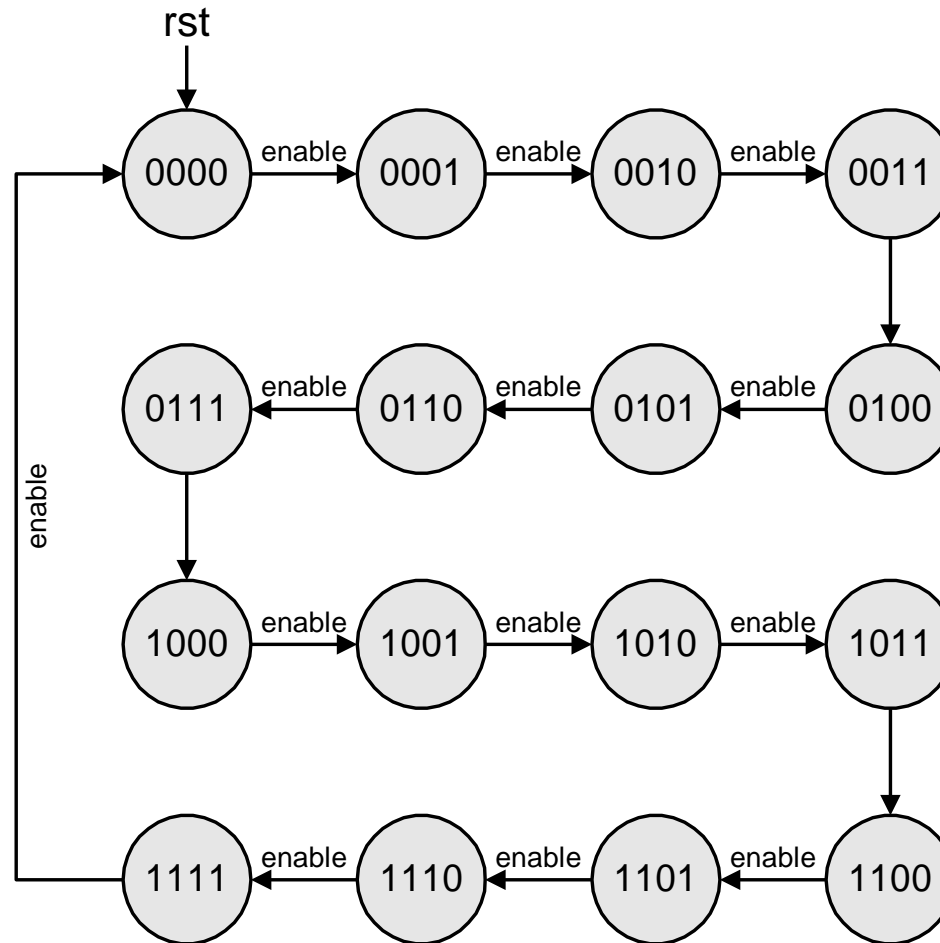


- Can this grow to larger counters?

Project Control

- Project is application oriented
 - Datapath and functional units designed to meet needs of instruction set
- Reduced complexity by splitting control / datapath.
- FSM allows for easy addition of operations
 - Allows use of single functional unit for multiple operations
- Use counters with FSM to reduce number of states
 - 1 Add state – use counter to determine when operation done

RISC Stored Program Machine (SPM)

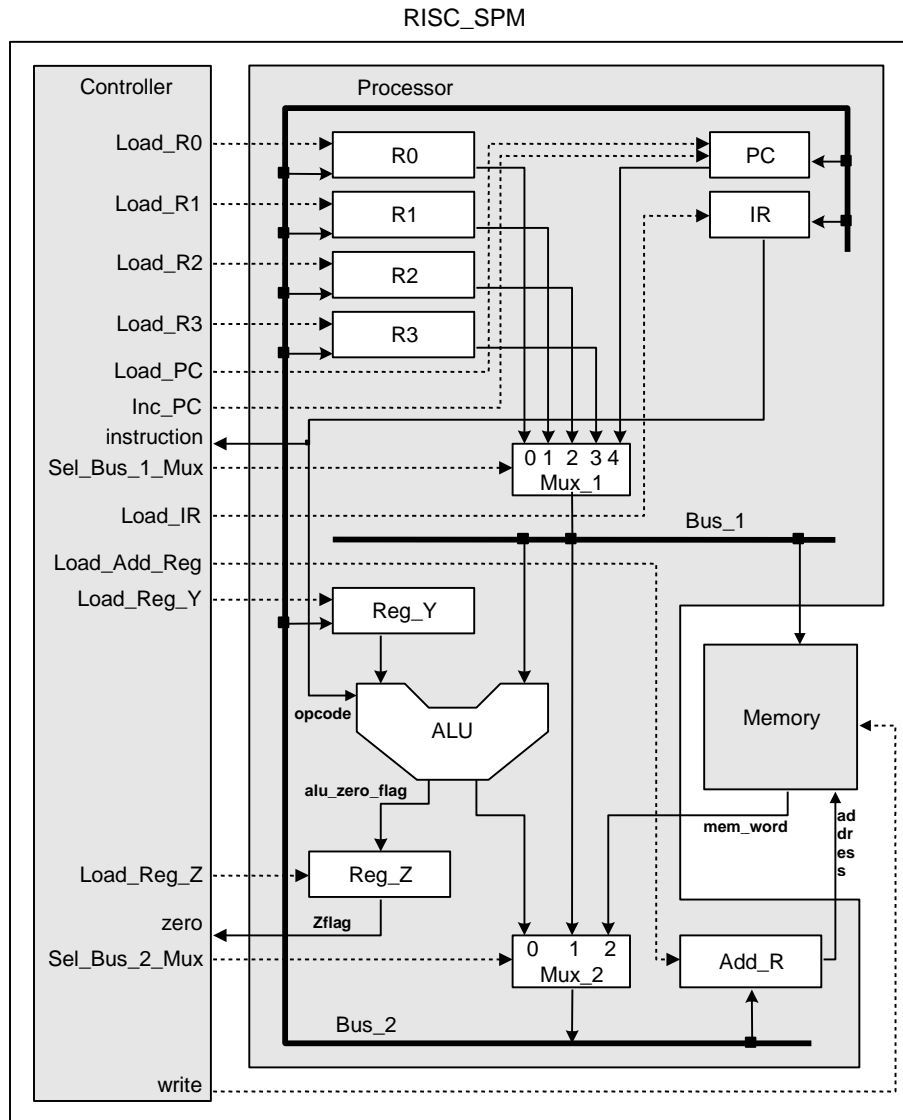

Instruction Sequence

- Fetch instruction from memory
- Decode instruction and fetch operands
- Execute instruction
 - ALU operations
 - Update storage registers
 - Update program counter (PC)
 - Update the instruction register (IR)
 - Update the address register (ADD_R)
 - Update memory
 - Control datapaths

Control Functions

- Functions of the control unit:
 - Determine when to load registers
 - Select the path of data through the multiplexers
 - Determine when data should be written to memory
 - Control the three-state busses in the architecture.

Control Signals

Control Signal

Load_Add_Reg

Load_PC

Load_IR

Inc_PC

Sel_Bus_1_Mux

Sel_Bus_2_Mux

Load_R0

Load_R1

Load_R2

Load_R3

Load_Reg_Y

Load_Reg_Z

write

Action

Loads the address register

Loads *Bus_2* to the program counter

Loads *Bus_2* to the instruction register

Increments the program counter

Selects among the *Program_Counter*, *R0*, *R1*, *R2*, and *R3* to drive *Bus_1*

Selects among *Alu_out*, *Bus_1*, and memory to drive *Bus_2*

Loads general purpose register *R0*

Loads general purpose register *R1*


Loads general purpose register *R2*

Loads general purpose register *R3*

Loads *Bus_2* to the register *Reg_Y*

Stores output of *ALU* in register *Reg_Z*

Loads *Bus_1* into the *SRAM* memory

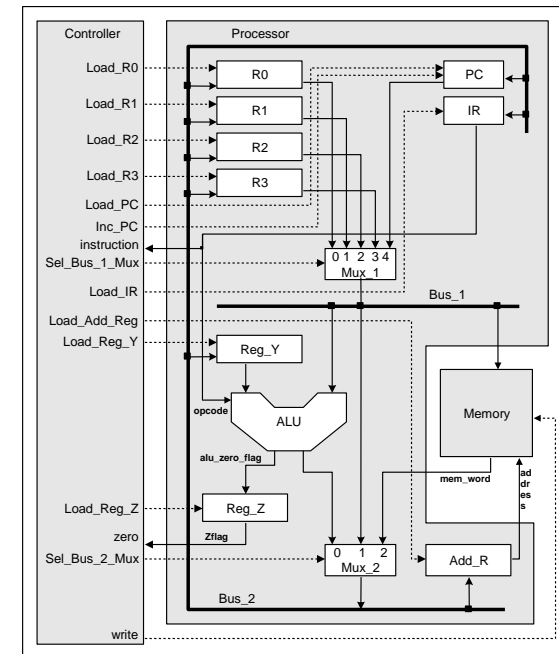

RISC SPM: Instruction Set [1]

- The design of the controller depends on the processor's instruction set.
- RISC SPM has two types of instructions.
- Short Instruction – 8 bits (basic arithmetic)

opcode				source		destination	
0	0	1	0	0	1	1	0

- Long Instruction – 16 bits (accessing memory)

opcode				source		destination	
0	1	1	0	1	0	don't care	don't care
address							
0	0	0	1	1	1	0	1

RISC SPM: Instruction Set [2]

Instr	Instruction Word			Action
	opcode	src	dest	
NOP	0000	??	??	none
ADD	0001	src	dest	dest \leftarrow src + dest
SUB	0010	src	dest	dest \leftarrow dest - src
AND	0011	src	dest	dest \leftarrow src && dest
NOT	0100	src	dest	dest \leftarrow ~src
RD*	0101	??	dest	dest \leftarrow memory[Add_R]
WR*	0110	src	??	memory[Add_R] \leftarrow src
BR*	0111	??	??	PC \leftarrow memory[Add_R]
BRZ*	1000	??	??	PC \leftarrow memory[Add_R]
HALT	1111	??	??	Halts execution until reset

* Requires a second word of data; ? denotes a don't care.

Controller Design

- Three phases of operation: *fetch*, *decode*, and *execute*.
 - Fetching: Retrieves an instruction from memory (2 clock cycles)
 - Decoding: Decodes the instruction, manipulates datapaths, and loads registers (1 cycle)
 - Execution: Generates the results of the instruction (0, 1, or 2 cycles)

Controller States [1]


- S_idle* State entered after reset is asserted. No action.
- S_fet1* Load the Add_R with the contents of the PC
- S_fet2* Load the IR with the word addressed by the Add_R,
Increment the PC
- S_dec* Decode the IR
Assert signals to control datapaths and register transfers.
- S_ex1* Execute the *ALU* operation for a single-byte instruction,
Conditionally assert the zero flag, Load the destination register

Controller States [2]


- S_rd1* Load Add_R with the second byte of an RD instruction
Increment the PC.
- S_rd2* Load the destination register with memory[Add_R]
- S_wr1* Load Add_R with the second byte of a WR instruction,
Increment the PC.
- S_wr2* Write memory[Add_R] with the source register
- S_br1* Load Add_R with the second byte of a BR instruction
Increment the PC.
- S_br2* Load the PC with the memory[Add_R]
- S_halt* Default state to trap failure to decode a valid instruction

Which states are similar?


Controller ASM: NOP/ADD/SUB/AND

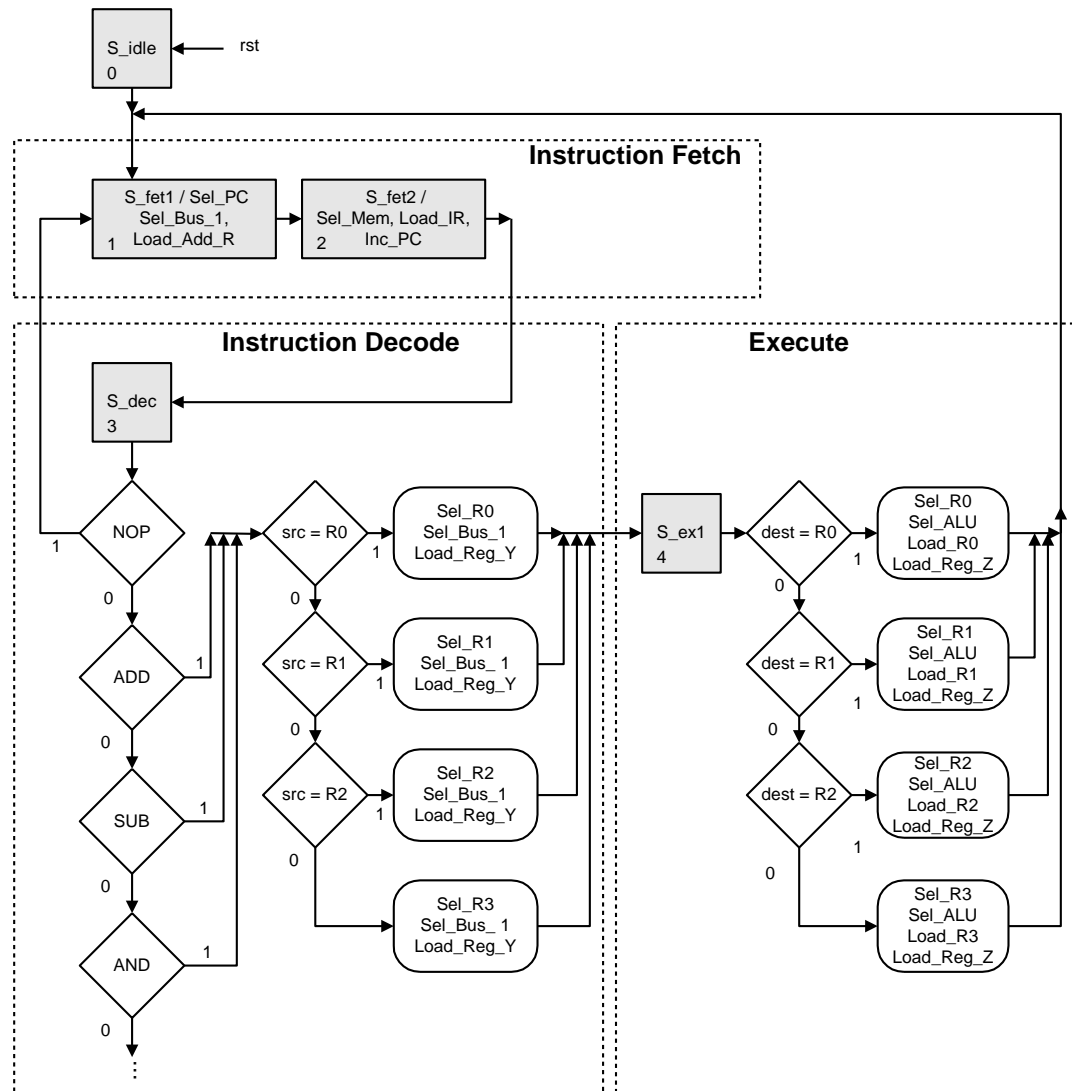


Controller ASM: NOT

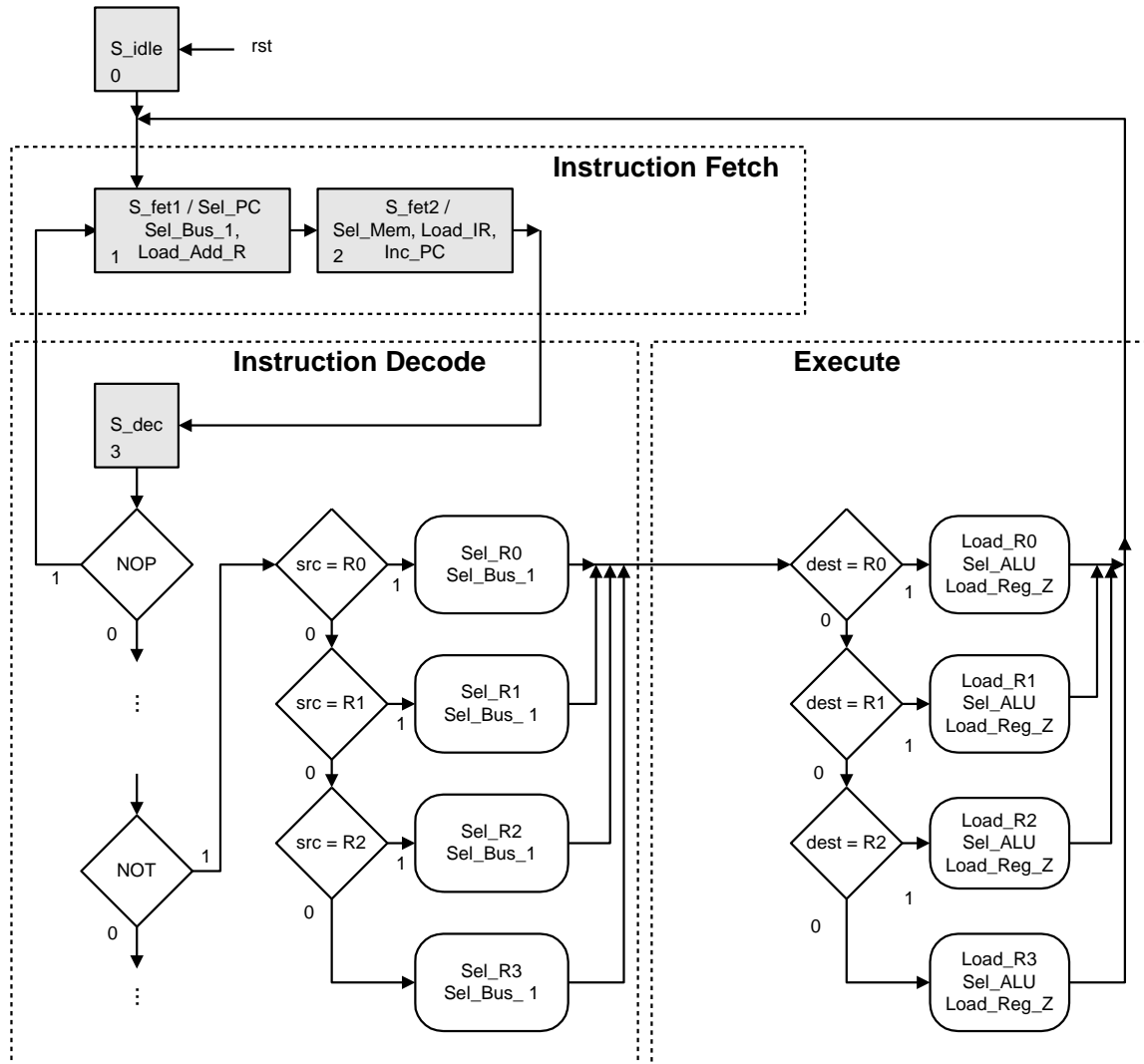


Controller ASM: RD

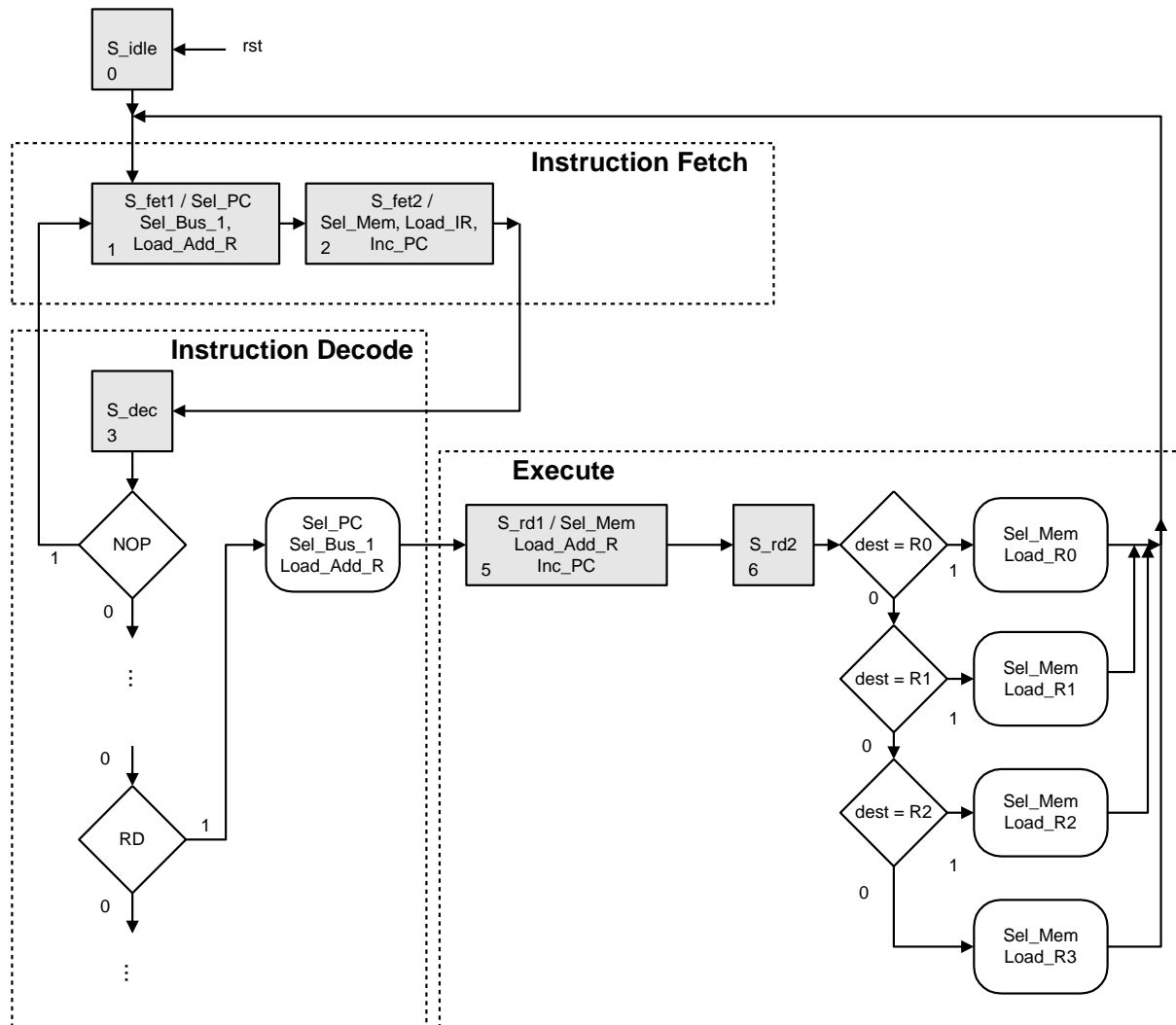

Controller ASM: WR

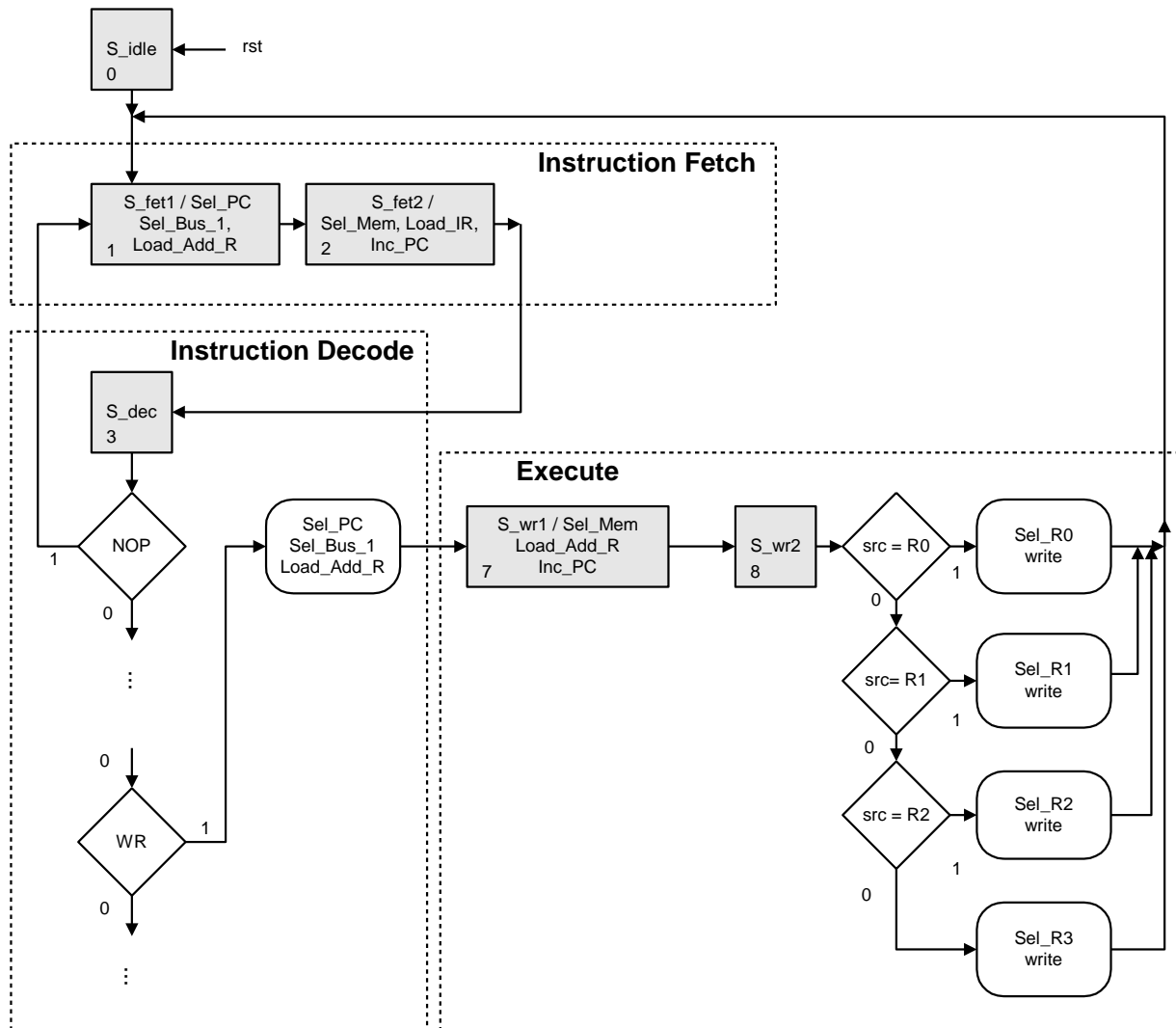

Controller ASM: BR/BRZ

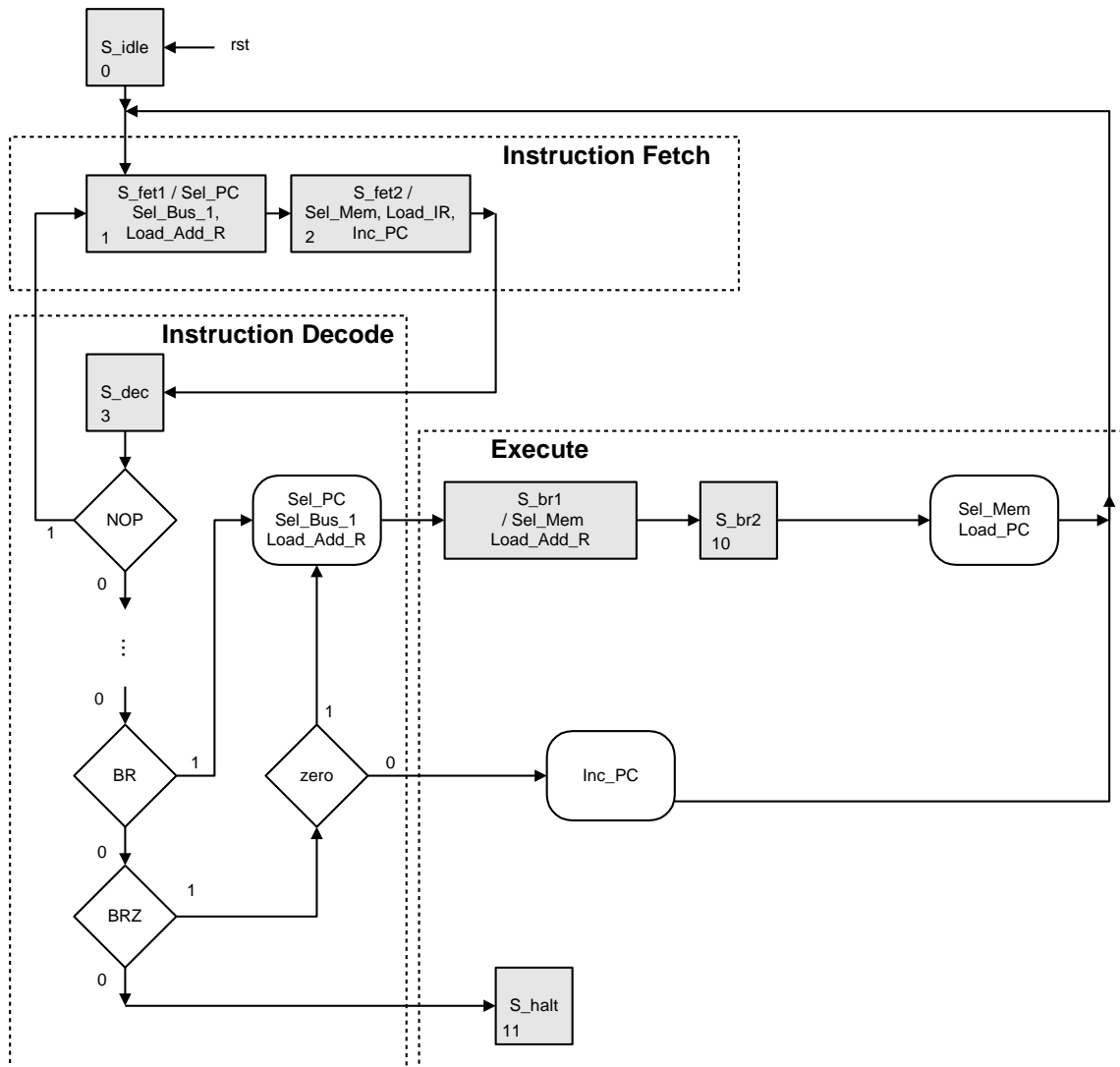

Questions on RISC SPM

- Why not include memory as part of the processing unit?
- How could the design be simplified?


Testing RISC SPM

- Clear the memory
- Load the memory with a simple program and data
- Execute simple program
 - Reads values from memory into registers
 - Perform subtraction to decrement a loop counter
 - Add register contents while executing the loop
 - Branch to a halt when the loop index is 0
- Probe memory locations and control signals to ensure correct execution

System on Chip (SoC)



From PCB to SoC

 

System on Chip cores

